

Post Lab 4

$$\textcircled{1} I_z = I_{z1} + I_{z2}$$

$$V_x - V_{x1} = I_x R$$

$$ILP \Rightarrow \begin{aligned} I_x^2 &= I_z I_{z1} \\ I_y^2 &= I_z I_{z2} \end{aligned}$$

\textcircled{a} All transistors should be forward active. The op-amps turn any input to (+) super negative because (-) is ground. So as long as V_x and V_y are just above 0, the drop across the resistor shouldn't turn it negative

\textcircled{b} The currents I_x , I_y , & I_z can be defined with ohm's law as $I_x = \frac{V_x}{R}$, $I_y = \frac{V_y}{R}$, & $I_z = \frac{V_z}{R}$ (\therefore)

$$\textcircled{c} KCL \Rightarrow I_z = I_{z1} + I_{z2}$$


$$\textcircled{d} I_x^2 = I_z I_{z1} \quad (ILP)$$

$$\textcircled{e} I_y^2 = I_z I_{z2}$$

$$\textcircled{f} \begin{aligned} I_x^2 + I_y^2 &= (I_z I_{z1}) + (I_z I_{z2}) \\ I_x^2 + I_y^2 &= I_z (I_{z1} + I_{z2}) \\ I_x^2 + I_y^2 &= I_z^2 \end{aligned}$$

$$I_z = \sqrt{I_x^2 + I_y^2}$$
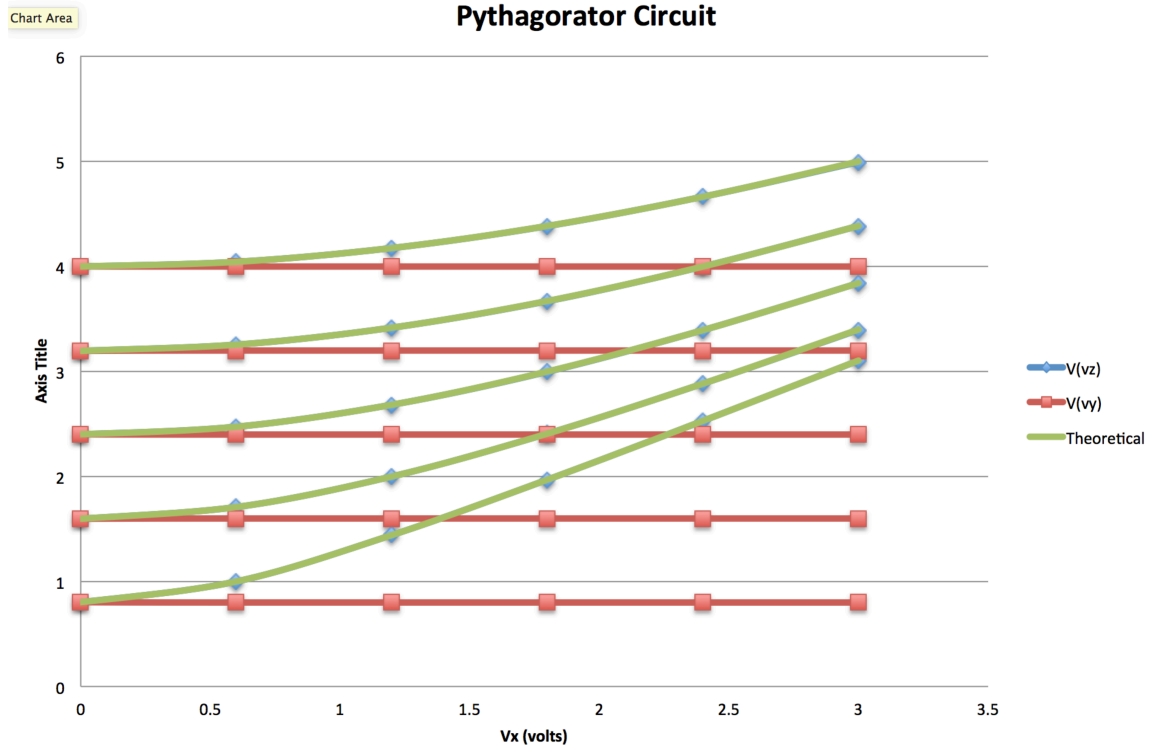
$$\textcircled{g} V_z = \sqrt{V_x^2 + V_y^2}$$



The circuit has exactly the behavior we expected as can be seen from the match on V_z and the theoretical fit of V_z